


## 13. Kirchoff's Law

### Background

Solution of linear systems can be applied to resistor network circuits. Kirchoff's voltage law says that the sum of the voltage drops around any closed loop in the network must equal zero. A closed loop has the obvious definition: starting at a node, trace a path through the circuit that returns you to the original starting node.
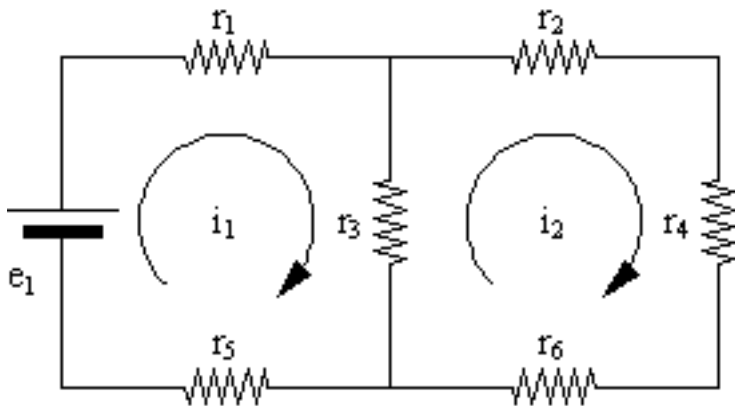
### Network #1

Consider the network consisting of six resistors and two battery, shown in the figure below.



There are two closed loops. When Kirchoff's voltage law is applied, we obtain the following linear system of equations.

$$(r_1 + r_3 + r_5) i_1 - r_3 i_2 = e_1$$

$$- r_3 i_1 + (r_2 + r_3 + r_4 + r_6) i_2 = 0$$

**Example 1.** Solve the network #1 for the currents  $i_1$ ,  $i_2$  given the following value for the resistors and battery:

$$r_1 = 10, r_2 = 10, r_3 = 10, r_4 = 20, r_5 = 10, r_6 = 30$$


and

$$e_1 = 20$$

**Solution 1.**
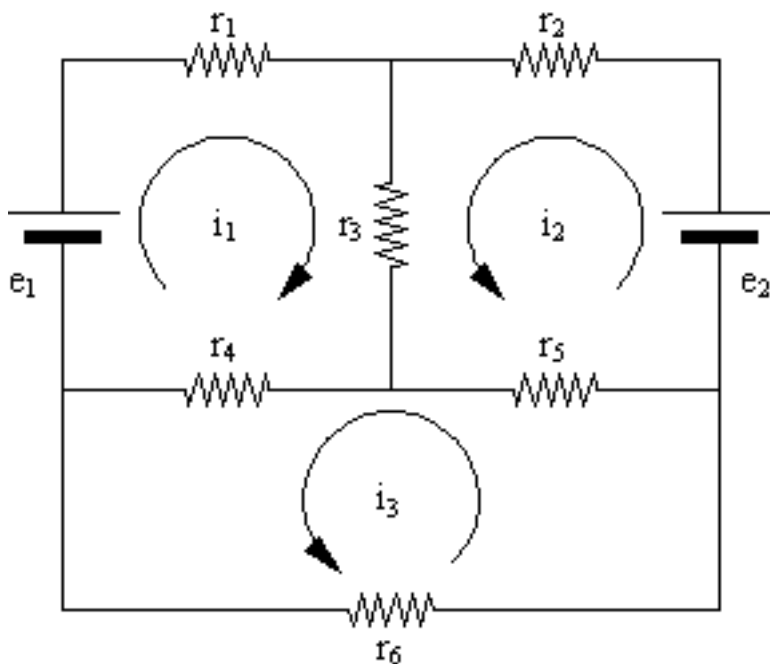
### Network #2

Consider the network consisting of six resistors and two batteries, shown in the figure below.



There are three loops. When Kirchoff's voltage law is applied, we obtain the following linear system of equations.

$$(r_1 + r_3 + r_4) i_1 + r_3 i_2 + r_4 i_3 = e_1$$

$$r_3 i_1 + (r_2 + r_3 + r_5) i_2 - r_5 i_3 = e_2$$

$$r_4 i_1 - r_5 i_2 + (r_4 + r_5 + r_6) i_3 = 0$$


**Example 2.** Solve the network #2 for the currents  $i_1$ ,  $i_2$ ,  $i_3$  given the following value for the resistors and batteries:

$$r_1 = 1, r_2 = 2, r_3 = 4, r_4 = 3, r_5 = 1, r_6 = 5$$

and

$$e_1 = 41, e_2 = 38$$

**Solution 2.**

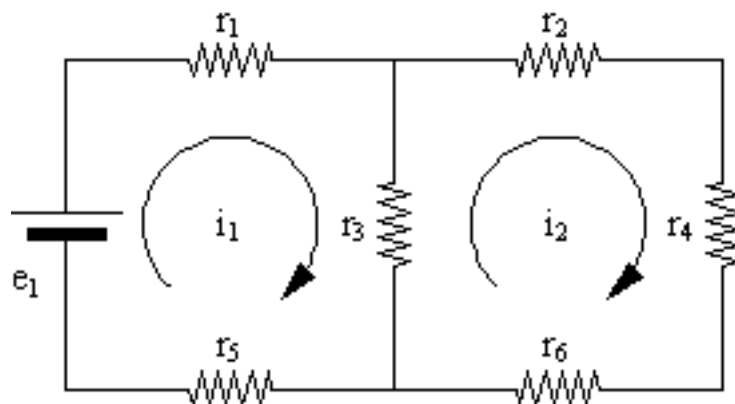

**Example 1.** Solve the network #1 for the currents  $i_1$ ,  $i_2$  given the following value for the resistors and battery:

$$r_1 = 10, r_2 = 10, r_3 = 10, r_4 = 20, r_5 = 10, r_6 = 30$$

and

$$e_1 = 20$$

**Solution 1.**

Solve the linear system

$$\begin{pmatrix} r_1 + r_3 + r_5 & -r_3 \\ -r_3 & r_2 + r_3 + r_4 + r_6 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} e_1 \\ 0 \end{pmatrix}$$

Solve the linear system

$$\begin{pmatrix} 30 & -10 \\ -10 & 70 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 20 \\ 0 \end{pmatrix}$$

The solution is

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} \frac{7}{10} \\ \frac{1}{10} \end{pmatrix} = \begin{pmatrix} 0.7 \\ 0.1 \end{pmatrix}$$

**Aside.** The solution could be found using Cramer's rule.

$$A = \begin{pmatrix} 30 & -10 \\ -10 & 70 \end{pmatrix}$$

$$B = \begin{pmatrix} 20 \\ 0 \end{pmatrix}$$

$$A_1 = \begin{pmatrix} 20 & -10 \\ 0 & 70 \end{pmatrix}$$

$$A_z = \begin{pmatrix} 30 & 20 \\ -10 & 0 \end{pmatrix}$$

$$i_1 = \text{Det}[\begin{pmatrix} 20 & -10 \\ 0 & 70 \end{pmatrix}] / \text{Det}[\begin{pmatrix} 30 & -10 \\ -10 & 70 \end{pmatrix}]$$

$$i_1 = (1400) / (2000)$$


$$i_1 = \frac{7}{10} = 0.7$$

$$i_z = \text{Det}[\begin{pmatrix} 30 & 20 \\ -10 & 0 \end{pmatrix}] / \text{Det}[\begin{pmatrix} 30 & -10 \\ -10 & 70 \end{pmatrix}]$$

$$i_z = (200) / (2000)$$

$$i_z = \frac{1}{10} = 0.1$$

## Network #2

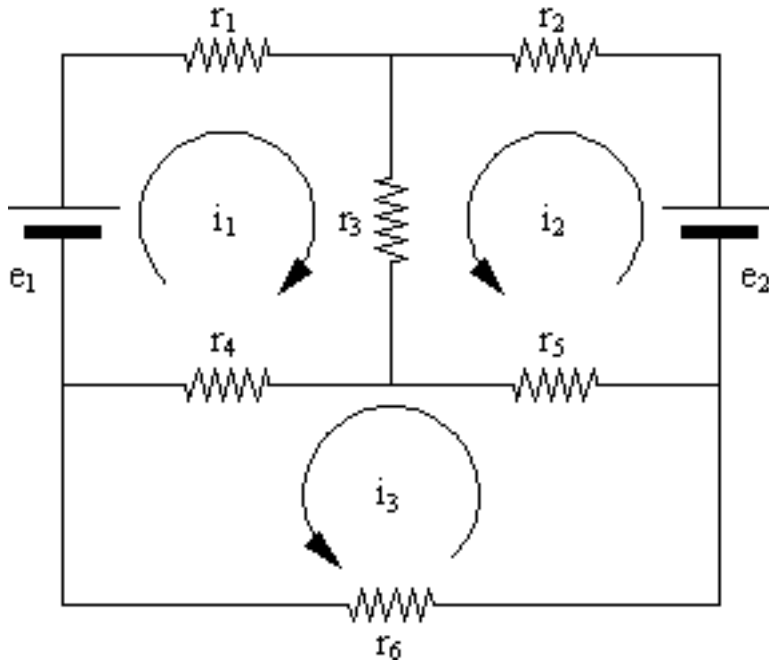

**Example 2.** Solve the network #2 for the currents  $i_1$ ,  $i_2$ ,  $i_3$  given the following value for the resistors and batteries:

$$r_1 = 1, r_2 = 2, r_3 = 4, r_4 = 3, r_5 = 1, r_6 = 5$$

and

$$e_1 = 41, e_2 = 38$$

**Solution 2.**

$$\begin{pmatrix} r_1 + r_3 + r_4 & r_3 & r_4 \\ r_3 & r_2 + r_3 + r_5 & -r_5 \\ r_4 & -r_5 & r_4 + r_5 + r_6 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} e_1 \\ e_2 \\ 0 \end{pmatrix}$$

Solve the linear system

$$\begin{pmatrix} 8 & 4 & 3 \\ 4 & 7 & -1 \\ 3 & -1 & 9 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 41 \\ 38 \\ 0 \end{pmatrix}$$

The solution is

$$\begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 4 \\ 3 \\ -1 \end{pmatrix} = \begin{pmatrix} 4. \\ 3. \\ -1. \end{pmatrix}$$

**Aside.** The solution could be found using Cramer's rule.

$$A = \begin{pmatrix} 8 & 4 & 3 \\ 4 & 7 & -1 \\ 3 & -1 & 9 \end{pmatrix}$$

$$B = \begin{pmatrix} 41 \\ 38 \\ 0 \end{pmatrix}$$

$$A_1 = \begin{pmatrix} 41 & 4 & 3 \\ 38 & 7 & -1 \\ 0 & -1 & 9 \end{pmatrix}$$

$$A_2 = \begin{pmatrix} 8 & 41 & 3 \\ 4 & 38 & -1 \\ 3 & 0 & 9 \end{pmatrix}$$

$$A_3 = \begin{pmatrix} 8 & 4 & 41 \\ 4 & 7 & 38 \\ 3 & -1 & 0 \end{pmatrix}$$

$$i_1 = \text{Det} \left[ \begin{pmatrix} 41 & 4 & 3 \\ 38 & 7 & -1 \\ 0 & -1 & 9 \end{pmatrix} \right] / \text{Det} \left[ \begin{pmatrix} 8 & 4 & 3 \\ 4 & 7 & -1 \\ 3 & -1 & 9 \end{pmatrix} \right]$$

$$i_1 = (1060) / (265)$$

$$i_1 = 4 = 4.$$

$$i_2 = \text{Det} \left[ \begin{pmatrix} 8 & 41 & 3 \\ 4 & 38 & -1 \\ 3 & 0 & 9 \end{pmatrix} \right] / \text{Det} \left[ \begin{pmatrix} 8 & 4 & 3 \\ 4 & 7 & -1 \\ 3 & -1 & 9 \end{pmatrix} \right]$$

$$i_2 = (795) / (265)$$

$$i_2 = 3 = 3.$$

$$i_3 = \text{Det} \left[ \begin{pmatrix} 8 & 4 & 41 \\ 4 & 7 & 38 \\ 3 & -1 & 0 \end{pmatrix} \right] / \text{Det} \left[ \begin{pmatrix} 8 & 4 & 3 \\ 4 & 7 & -1 \\ 3 & -1 & 9 \end{pmatrix} \right]$$

$$i_3 = (-265) / (265)$$

$$i_3 = -1 = -1.$$